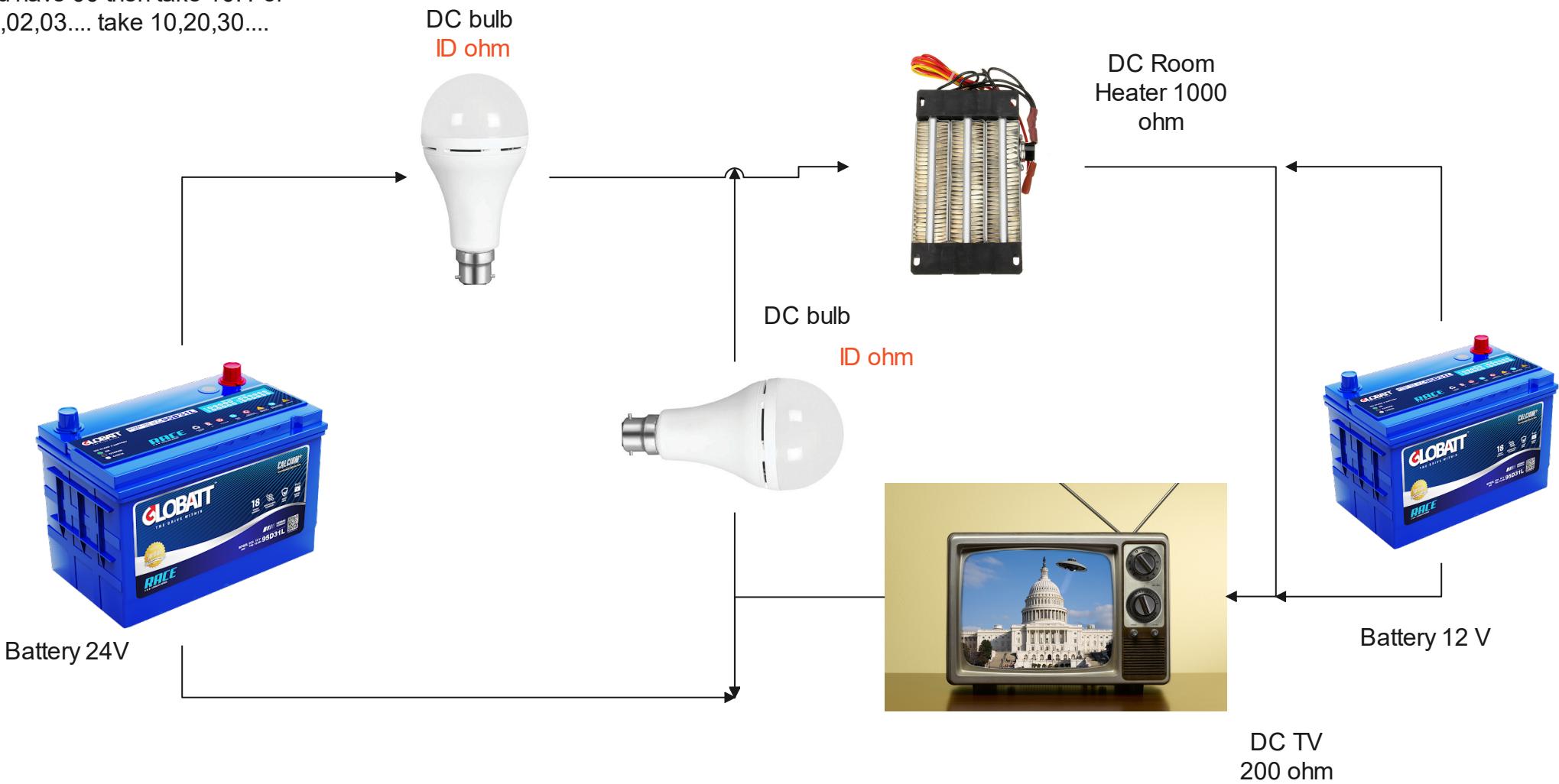


ID ohm here use last 2 digit of ID.
Like for 15-23456-1; ID =56... IF
you have 00 then take 10. For
01,02,03.... take 10,20,30....



In this circuit consider DC Room Heater as a load. Find out how much current and voltage flowing through heater by using superposition, thevenin and Norton theory also prove this circuit follow KCL theory. Show your calculation in theory and simulation by multisim.